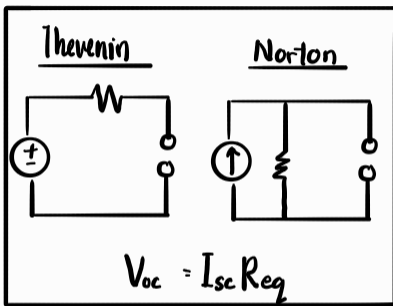


$$V_{out} = V_{in} \cdot \left(\frac{R_{out}}{R_{total}} \right)$$

$$I_{out} = I_{total} \cdot \left(\frac{R_{total}}{R_{out}} \right)$$




1st order circuits [RC / LC circuit]

$$\tau = RC \text{ or } L/R \quad V_c(\infty) \text{ [Steady state } t = 5\tau]$$

$$V_c(t) = k_1 e^{-t/\tau} + k_2$$
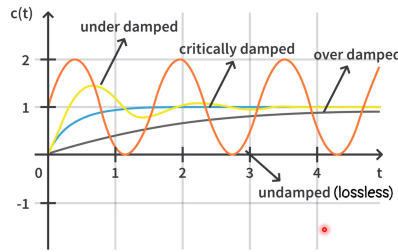
$$i_L(t) = k_1 e^{-t/\tau} + k_2 \quad i_L(\infty)$$



1st order circuits (RLC circuits)

- 1) Make eqn only have 1 dependent & independent variable
- 2) Make it into 1st order ODE w/ highest order coeff. 1.
- 3) Convert to Characteristic Eqn

$$V_L = L \frac{di_L(t)}{dt}$$

$$I(t) = \frac{1}{L} \int_0^t V_L(t) dt + V_L(0)$$

$$i_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_0^t i_C(t) dt + V_C(0)$$

$$\textcircled{1} \frac{d^2 f(t)}{dt^2} + 2\alpha \frac{df(t)}{dt} + \omega_0^2 f(t) = 0$$

Damping constant

- 1) Parallel RLC = $\frac{1}{2RC}$
- 2) Series RLC = $\frac{R}{2L}$

[Decay tendency]

Undamped Natural Freq.

$1/\sqrt{LC}$ for parallel & series RLC

[Oscillation tendency]

$$\textcircled{2} s^2 + 2\alpha s + \omega_0^2 = 0 \quad ; \quad s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

[Characteristic Eqn]

$$\textcircled{3} \frac{d^2 f(t)}{dt^2} + 2\omega_0 \zeta \frac{df(t)}{dt} + \omega_0^2 f(t) = 0$$

Damping ratio

$$\zeta = \alpha / \omega_0 = \frac{R/\sqrt{L/C}}{1/\sqrt{LC}}$$

[Normalized damping]

$$\textcircled{4} \frac{df(t)}{dt} + \frac{\omega_0}{Q} \frac{df(t)}{dt} + \omega_0^2 f(t) = 0$$

Quality factor

$$\text{parallel} = \omega_0 RC$$

$$\text{series} = \omega L/R$$

[Energy-preserving tendency]

Parallel $\alpha = \frac{1}{2RC}$ Series $\alpha = R/2L$	OVERDAMPED	CRITICALLY DAMPED	UNDERDAMPED	LOSSLESS
Roots	Both real & negative	Equal, real & negative	Complex conjugate	Imaginary
s_1, s_2	$-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$-\alpha, -\alpha$	$-\alpha \pm j\omega_d$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$\pm j\omega_0$
Damping const α	$\alpha > \omega_0$	$\alpha = \omega_0$	$0 < \alpha < \omega_0$	$\alpha = 0$
Quality factor Q	$0 < Q < 0.5$	$Q = 0.5$	$Q > 0.5$	$Q \rightarrow \infty$
Damping ratio ζ	$\zeta > 1.0$	$\zeta = 1.0$	$0 < \zeta < 1.0$	$\zeta = 0$
homogenous response (series & parallel)	$k_1 e^{s_1 t} + k_2 e^{s_2 t}$	$(k_1 + k_2 t) e^{-\alpha t}$	$k_1 e^{-\alpha t} \cos(\omega_d t) + k_2 e^{-\alpha t} \sin(\omega_d t)$	

$$A \angle \phi = A \cos(\omega t + \phi) = A e^{j\phi}$$

$$\sin \theta = \cos(\theta - 90^\circ)$$


$$\cos \theta = \sin(\theta + 90^\circ)$$

$$Z = R + jX \text{ [Final ans: Complex form]}$$

$$\text{Capacitor, } Z_C = -j \frac{1}{\omega C}$$

$$\text{Inductor, } Z_L = j\omega L$$

Source transformation

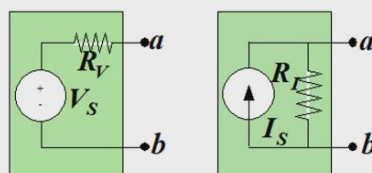

Improved model for voltage source

Improved model for current source

Advance AC S.S Analysis

① Mesh (loop w no other loop inside it) analysis

- 1) Draw mesh current [usually clockwise]
- 2) Write KVL for every mesh current
- 3) Solve simultaneous eqn

② Nodal Branch (≥ 3 wires connected to node) analysis

- 1) Find all node branch w more than 3 wires
- 2) Write KCL eqn for every node
- 3) Solve simultaneous eqs

③ Unit current method

- 1) Assume 1A flow through the wanted output

2) Then use $\frac{V_{\text{output}}}{V_{\text{source}}} = \frac{V_{\text{output (unit)}}}{V_{\text{source (unit)}}}$ ⓐ $\frac{I_{\text{output}}}{V_{\text{source}}} = \frac{I_{\text{output (unit)}}}{V_{\text{source (unit)}}}$

$$\frac{I_{\text{output}}}{I_{\text{source}}} = \frac{I_{\text{output (unit)}}}{I_{\text{source (unit)}}} \quad \text{ⓑ} \quad \frac{V_{\text{output}}}{I_{\text{source}}} = \frac{V_{\text{output (unit)}}}{I_{\text{source (unit)}}}$$

Power Factor Correction

Without capacitor :

$$S_{\text{old}} = P_{\text{old}} + jQ_{\text{old}} = |S_{\text{old}}| \angle \theta_{\text{old}}$$

$$pf_{\text{old}} = \cos(\theta_{\text{old}})$$

With capacitor

$$S_{\text{new}} = S_{\text{old}} + S_{\text{capacitor}}$$

$$= P_{\text{old}} + jQ_{\text{old}} - jQ_{\text{capacitor}}$$

$$= |S_{\text{new}}| \angle \theta_{\text{new}}$$

$$pf_{\text{new}} = \cos(\theta_{\text{new}})$$

$$Q_{\text{capacitor}} = |V_L| |I_{\text{capacitor}}|$$

$$= |V_L|^2 \omega C$$

$$\tan \theta_{\text{new}} = \frac{Q_{\text{old}} - Q_{\text{capacitor}}}{P_{\text{old}}}$$

$\text{+ve} = \text{consumed}$, $\text{-ve} = \text{supplied}$ $V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$, $I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$, $X_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} [x(t)]^2 dt}$

Instantaneous Power, $P(t) = \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$

Avg / Real Power, $P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = (V_{\text{rms}})(I_{\text{rms}}) \cos(\theta_v - \theta_i) = |S| \cos \theta_z$


Max avg Power, $P_{\text{max}} = \frac{1}{2} \left[\frac{|V_{\text{oc}}|^2}{4 R_{\text{thvenin}}} \right]$, where $Z_{\text{thvenin}} = R_{\text{thvenin}} + jX_{\text{thvenin}}$

Complex Power, $S = (V_{\text{rms}})(I_{\text{rms}})^* = (V_{\text{rms}})(I_{\text{rms}}) \angle \theta_v - \theta_i = P + jQ$

$$|S| = \sqrt{P^2 + Q^2} = (V_{\text{rms}})(I_{\text{rms}}) = |I_{\text{rms}}|^2 Z$$

$$P = |I_{\text{rms}}|^2 R, \quad Q = |I_{\text{rms}}|^2 X$$

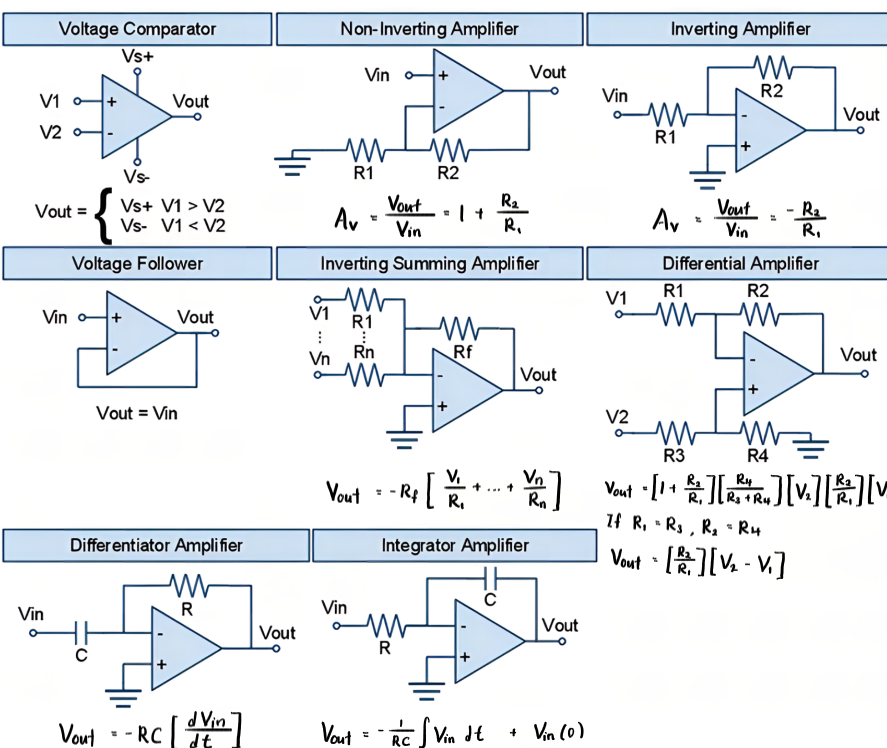Basic Operational Amplifier Configurations



MOSFET

$V_{\text{GS}} < V_{\text{th}}$ [cutoff]	
$V_{\text{GS}} > V_{\text{th}}$ $V_{\text{DS}} < V_{\text{GS}} - V_{\text{th}}$ [Triode]	
$V_{\text{GS}} > V_{\text{th}}$ $V_{\text{DS}} > V_{\text{GS}} - V_{\text{th}}$ [Saturation]	

BJT

$V_{\text{BE}} < V_{\text{th}}$	$I_c = 0$	Cutoff
$V_{\text{BE}} \approx V_{\text{th}}$ $V_{\text{CE}} \geq V_{\text{BE}}$	$I_c = \beta I_B$	Forward Active
$V_{\text{BE}} \approx V_{\text{th}}$ $V_{\text{CE}} \leq V_{\text{BE}}$	$I_c < \beta I_B$	Saturation