

Fundamentals

1) Voltage, V is always a defined difference

$$V_{\text{element}} = V(+ \text{ terminal of element}) - V(- \text{ terminal of element})$$

2) Voltages labelled at nodes [Node voltage] always has its node as the +ve terminal

$$\begin{aligned} V_{\text{node}} &= V(+) - V(-) \\ &= V(\text{node}) - V(\text{reference node}) \quad \text{most of the time ground} \\ &= V(\text{node}) - 0 \end{aligned}$$

3) Polarity of elements of unknown voltage can be chosen arbitrarily

You can always choose a reference direction for a variable voltage, V

If your assumed polarity is opposite to reality, the calc. voltage will be negative.

3) Current direc. can be chosen arbitrarily for an unknown current

You can always choose a reference direction for a variable current, I

If your assumed direc. is opposite to reality, the calc. current will be negative.

4) $V_{\text{element}} = IR$ only works under $\text{current enters } + \text{ terminal}$ passive sign convention, otherwise $V = -IR$
current enter - terminal

5) KVL sign depends on how you cross the polarity, not current.

Crossing + to - give $-V$, lose potential
Crossing - to + give $+V$, gain potential

} Normal convention
but can
be vice versa.

[Just be consistent]


Example using rule 1, 2, 3, 4

chosen arbitrarily

given

But not 2A cuz its not a variable

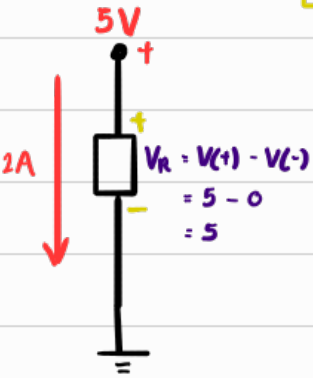We can choose the polarity of V_R arbitrarily




Since current in +,

$$V_R = IR$$

$$5 = 2R$$

$$R = 2.5 \Omega$$

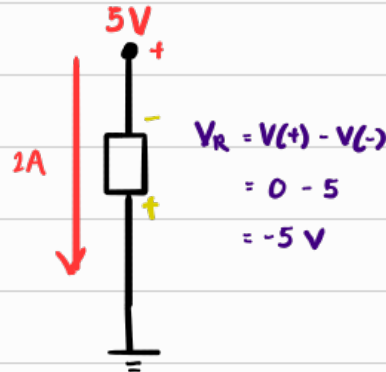


Since current in -

$$V_R = -IR$$

$$-5 = -2R$$

$$R = 2.5 \Omega$$

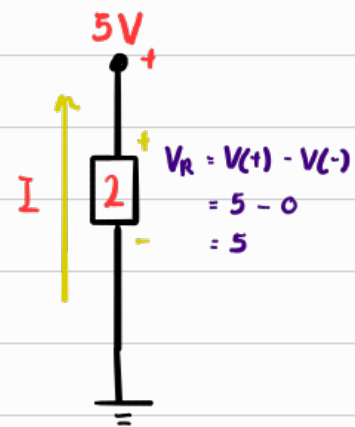We can choose direc of I & polarity of V_R arbitrarily




Since current in -

$$V_R = -IR$$

$$5 = -I(2)$$

$$I = -2.5 \text{ V}$$

$$= 2.5 \text{ downwards}$$

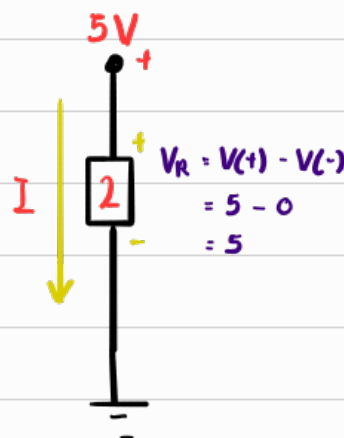


Since current in +

$$V_R = IR$$

$$5 = I(2)$$

$$I = 2.5 \text{ V}$$

$$= 2.5 \text{ downwards}$$

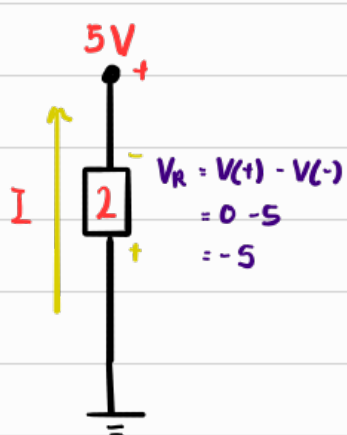


Since current in +

$$V_R = IR$$

$$-5 = I(2)$$

$$I = -2.5 \text{ V}$$

$$= 2.5 \text{ downwards}$$

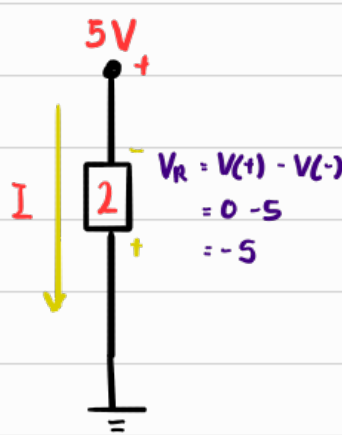

Since current in +


$$V_R = -IR$$

$$-5 = -I(2)$$

$$I = 2.5 \text{ V}$$

$$= 2.5 \text{ downwards}$$

Extra Example

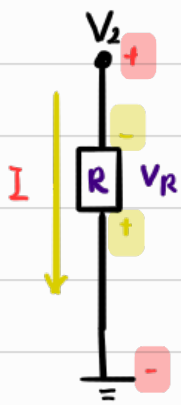

$$V_R = V(+) - V(-)$$

$$V_R = 0 - V_2$$

$$V_R = -V_2$$

$$= -(IR)$$

$$V_R = -IR \quad \text{--- ①}$$

Take Note:
 $V_2 \neq -IR$
 because I flows
 from V_2^+ to V_2^-

$$V_R = -IR \quad \text{--- ②}$$

Take Note:
 I flows from
 V_R^- to V_R^+

